


Challenges of SSB

The development of the QSX All-mode HF transceiver kit

QRP ARCI FDIM seminar

Thursday 16-May-2019

Hans Summers, G0UPL

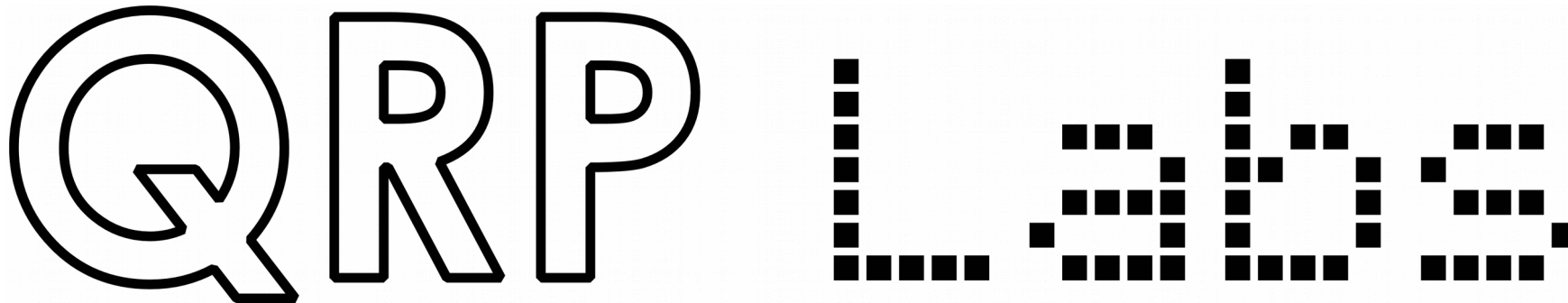

<http://qrp-labs.com>

QSX transceiver kit


- QRP Labs **S**SB/CW **X**cvr
- Introduced at YOTA 2018 summer buildathon in S.Africa
- Still under development
- AIM:
 - Very high performance HF transceiver
 - 160m to 10m, all-mode, 10W
 - Very low cost
 - Tons of features
 - Easy, fun and education to build and use

COMING SOON




QCX 5W CW transceiver kit

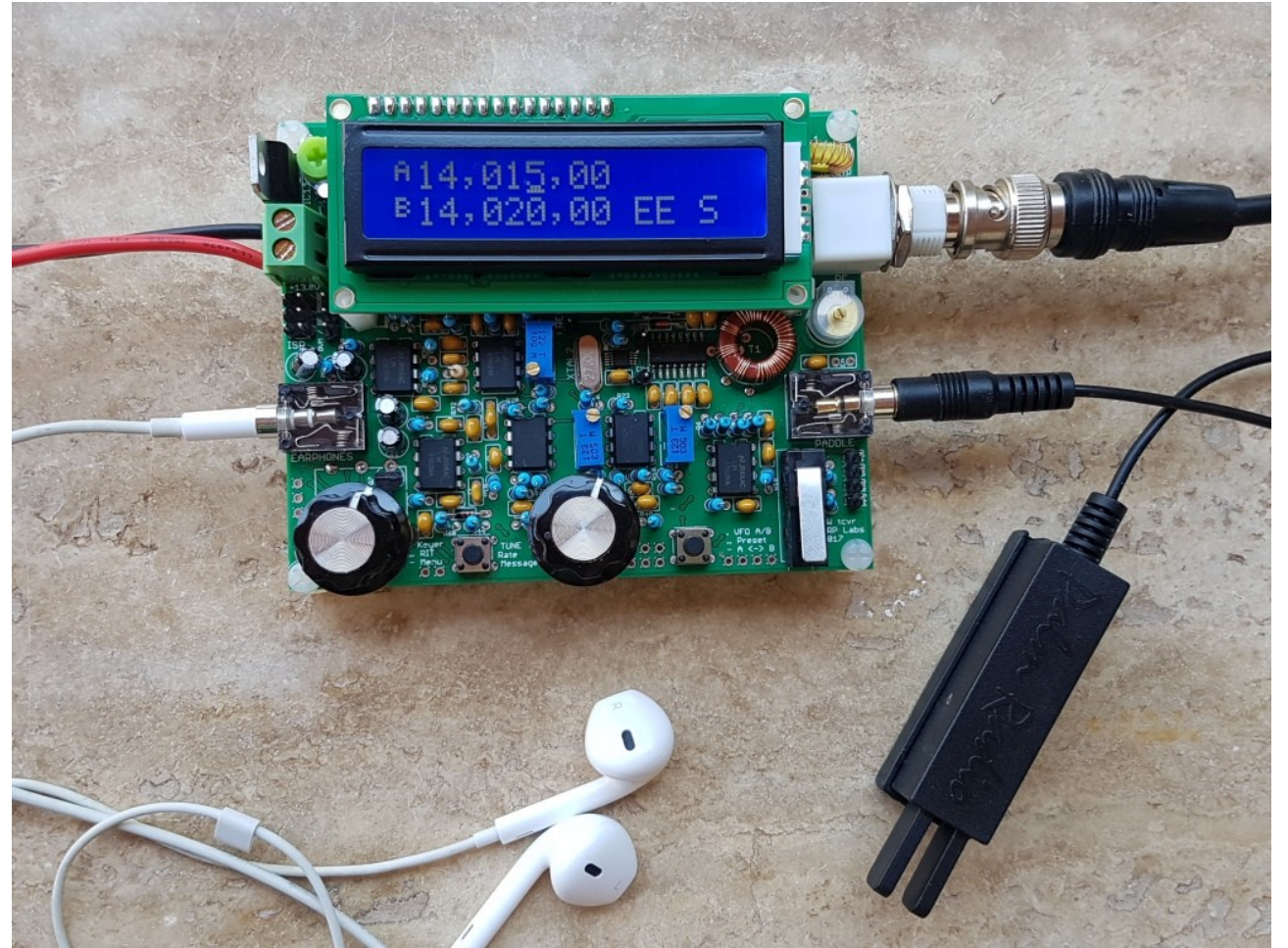- QRP Labs CW Xcvr
- Introduced at YOTA 2017 summercamp buildathon
- Since 21-Aug-2017, 7,230 kits shipped
- Mono-band CW transceiver with high performance, built-in test equipment, and loads of features



Transceiver architecture

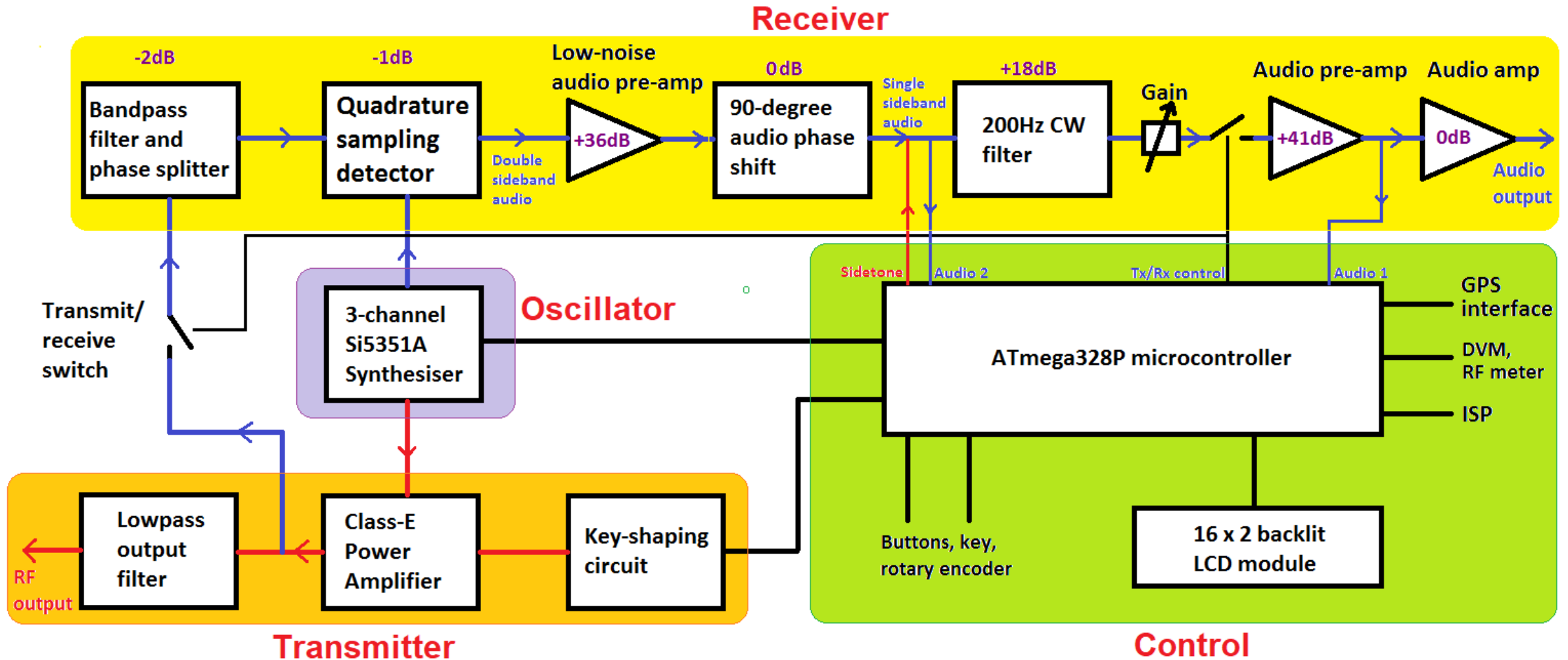- This is the old QCX 5W CW architecture... a good starting point for SSB?



Problems adapting that for SSB

Receiver:

- Audio phase shift must be wideband and accurate
- We're going to want AGC
- Multiple filters, for SSB and for CW and perhaps different filter widths
- More complex Band Pass Filter because we want it to be multi-band

Transmitter:

- For CW, the PA is easy (Class C, D, E are all Ok)... but for SSB we need a Linear - much more complex
- We need a proper SSB exciter, not just an oscillator feeding an amp
- We're going to want Speech processing
- Must handle CW key-shaping too

Software Defined Radio (SDR) to the rescue

SDR replaces some of the blocks of the radio transceiver with Digital Signal Processing by a computer

- Advantages:
 - Lots of flexibility to implement features
 - Software can be updated to easily add new features
 - Cost savings
- Disadvantages:
 - Requires a computer!
 - Requires high performance conversion between digital and analog
 - Digital Signal Processing sounds scary



SDR: solving the disadvantages

1. Requires a computer

- Use an embedded 32-bit ARM processor!
- STM32 series are popular, easy and low cost
- Plenty of processing power, at 168MHz



2. Requires high performance conversion between digital and analog

- 24-bit ADC and DAC chips are available
- Cost of Processor an ADC and DAC chip is LESS than the analog circuits they replace
- Some of the conversions can use the built-in 12-bit ADC and DAC in the processor



3. Digital Signal Processing sounds scary

- Lots of examples around the internet!




QSOX Block diagram

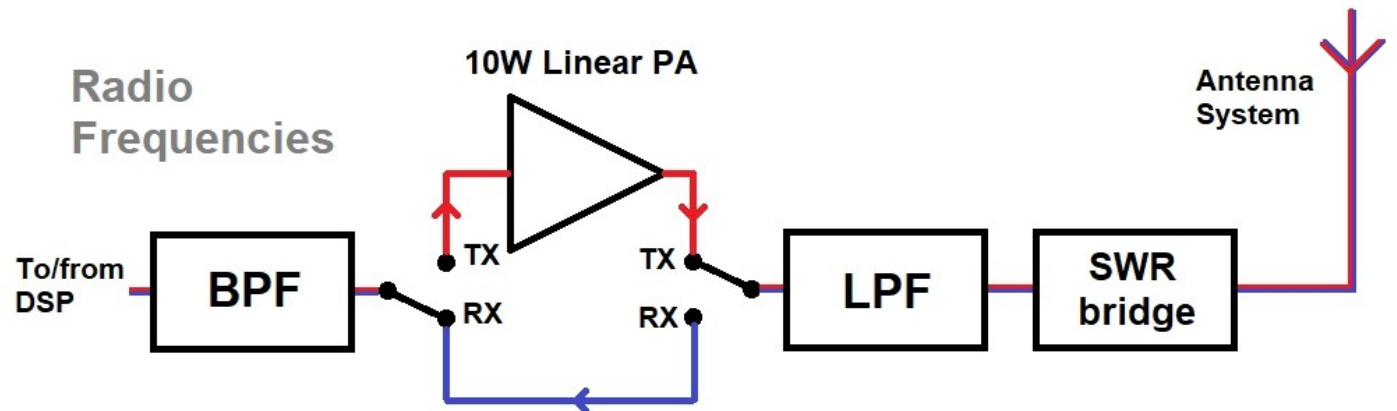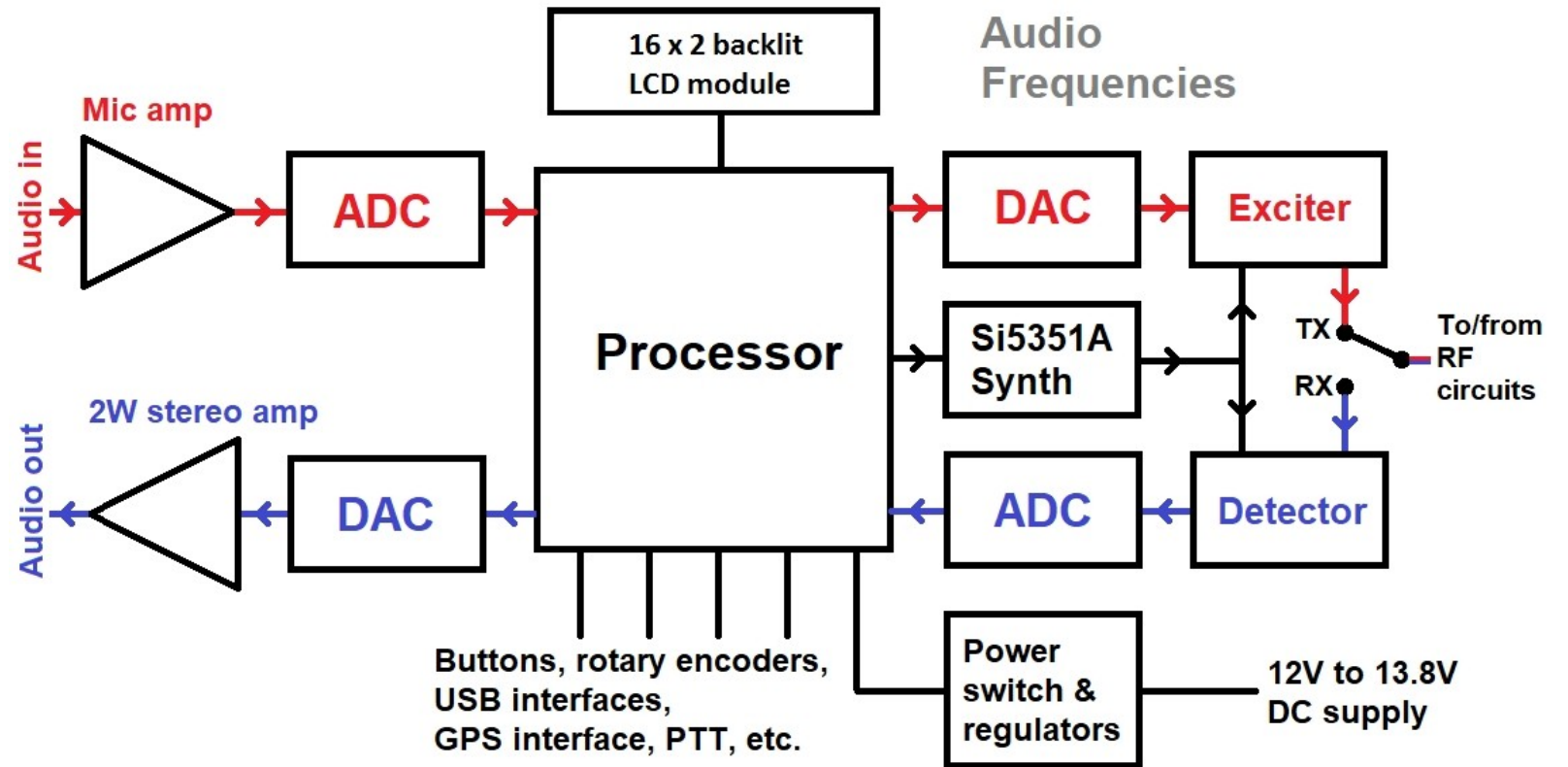- Key point: the cost of ADC + DAC + Processor is LESS than the analog circuit blocks they replace!



QSX features

- DSP (filters, AGC, Speech compression, noise reduction)
- Built-in test and alignment equipment
- SWR Bridge
- USB A and USB B connectors
- Paddle input for CW (built-in IAMBIC keyer)
- WSPR and QRSS modes beacon mode included
- GPS interface for frequency and time discipline, and beacon modes
- RJ45 connector for Kenwood/Yaesu style microphones
- Realtime clock (CR2032 battery holder)
- 10W power output CW, Digital or SSB

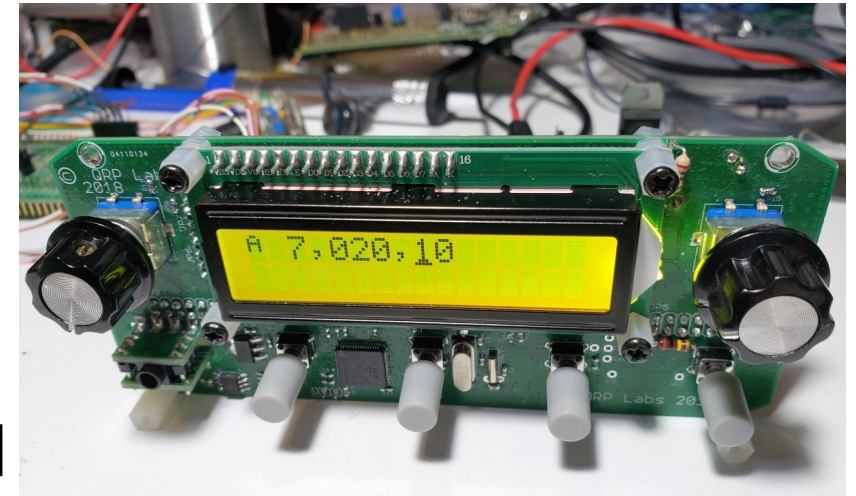

CW and SSB features

CW features

- Full or Semi-breakin (QSK)
- Laminar keyer
- On-screen CW decoder
- Message and frequency memories
- Full 10W Power output
- Raised-cosine envelope shaping
- Variable filter centre frequency and bandwidth

• SSB Features

- Automatic Gain Control (AGC)
- Speech processing/compression
- Variable bandwidth filters
- 10W PEP power output
- Dual mic




Digital and other modes support

- RTTY and PSK31 supported natively (no PC required)
 - USB keyboard text entry
 - CW to RTTY/PSK31 translator
 - RTTY and PSK31 decoding on-screen
- Connect to a PC with a common USB cable, for:
 - Digital modes: USB 24-bit USB soundcard emulation
 - Virtual Serial COM port, for CAT rig control over the **same** USB cable
- Full 10W Power output continuous key-down (100% duty cycle)
- Also AM, FM modes

Performance


- Around 100dB dynamic range expected
- 24-bit Receiver ADC has 110dB dynamic range
- High IP3 front end mixer (Quadrature Sampling Detector)
- 12kHz IF mode (away from mains hum)
- Narrow Band Pass Filter per band, attenuates out-of-band signals
- Compliant with all regulations on harmonic and spurious output
- Good IMD transmit performance
- Variable transmitter power output 1 to 10W
- DSP features: sharp filters, noise reduction, notch filter etc.

Quadrature Sampling Detector

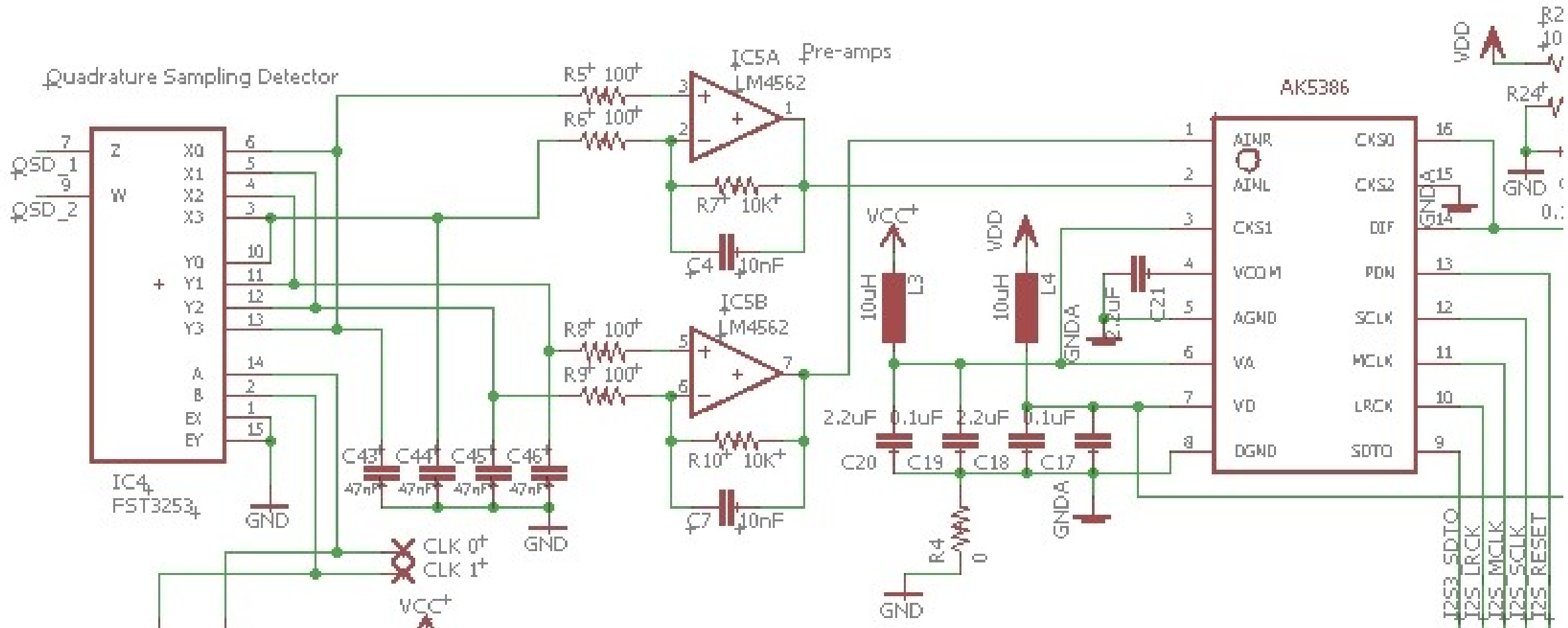


Mechanical design

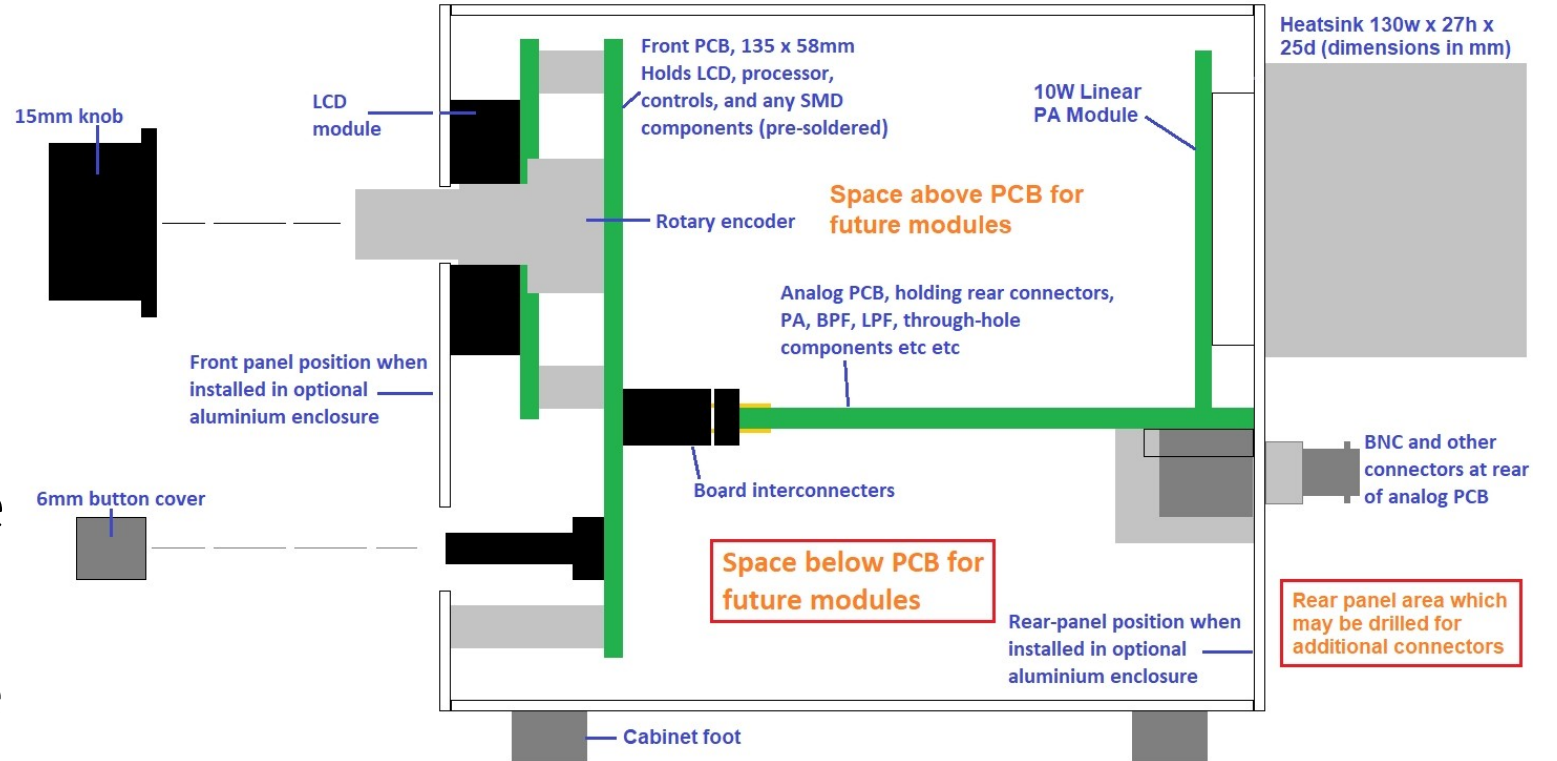
- Think about the enclosure
- Think about manufacturing process
- Controls should all be at the right altitude
- All controls should be board-mounted to remove any wiring




Rear board and PA board

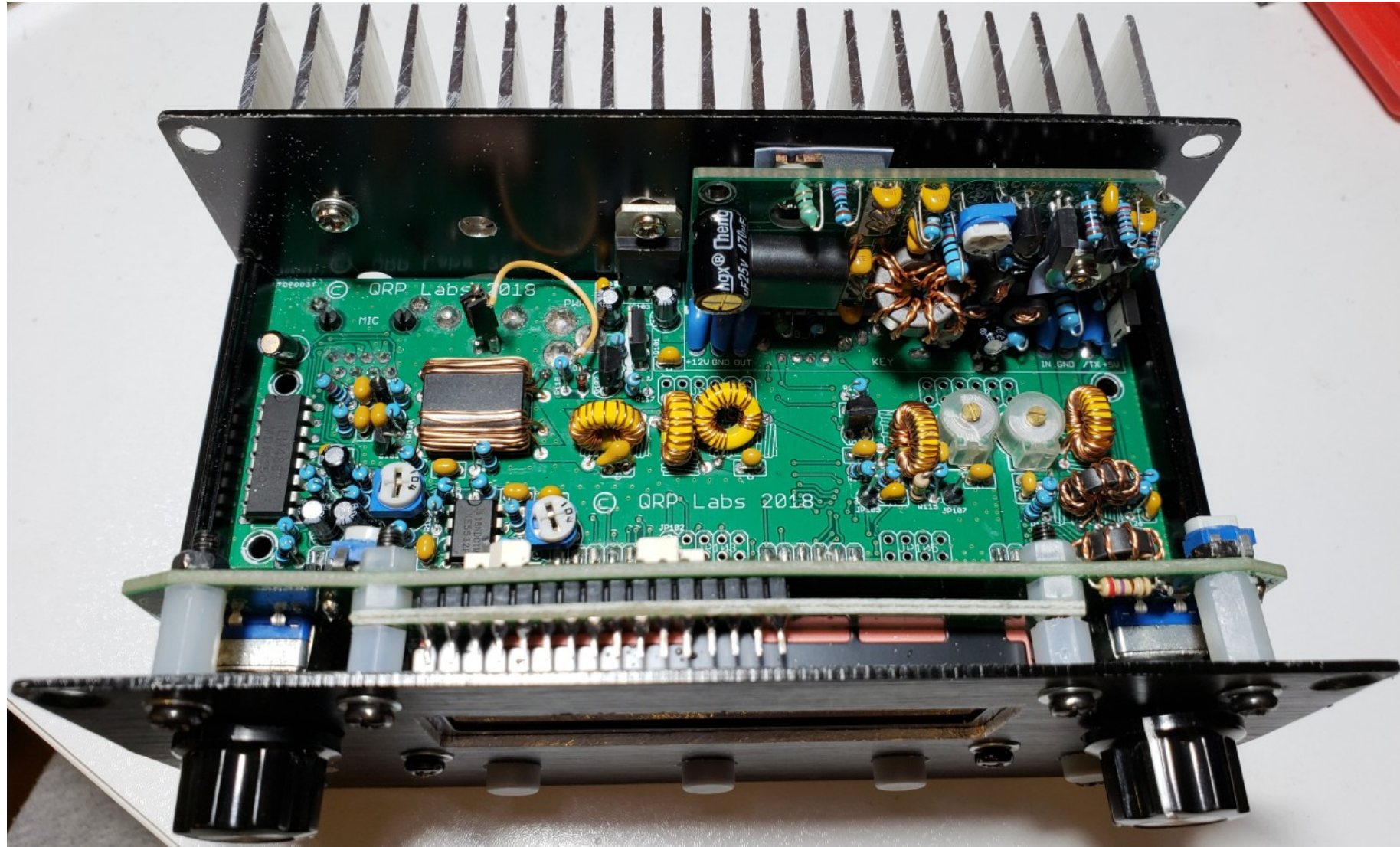

Enclosure

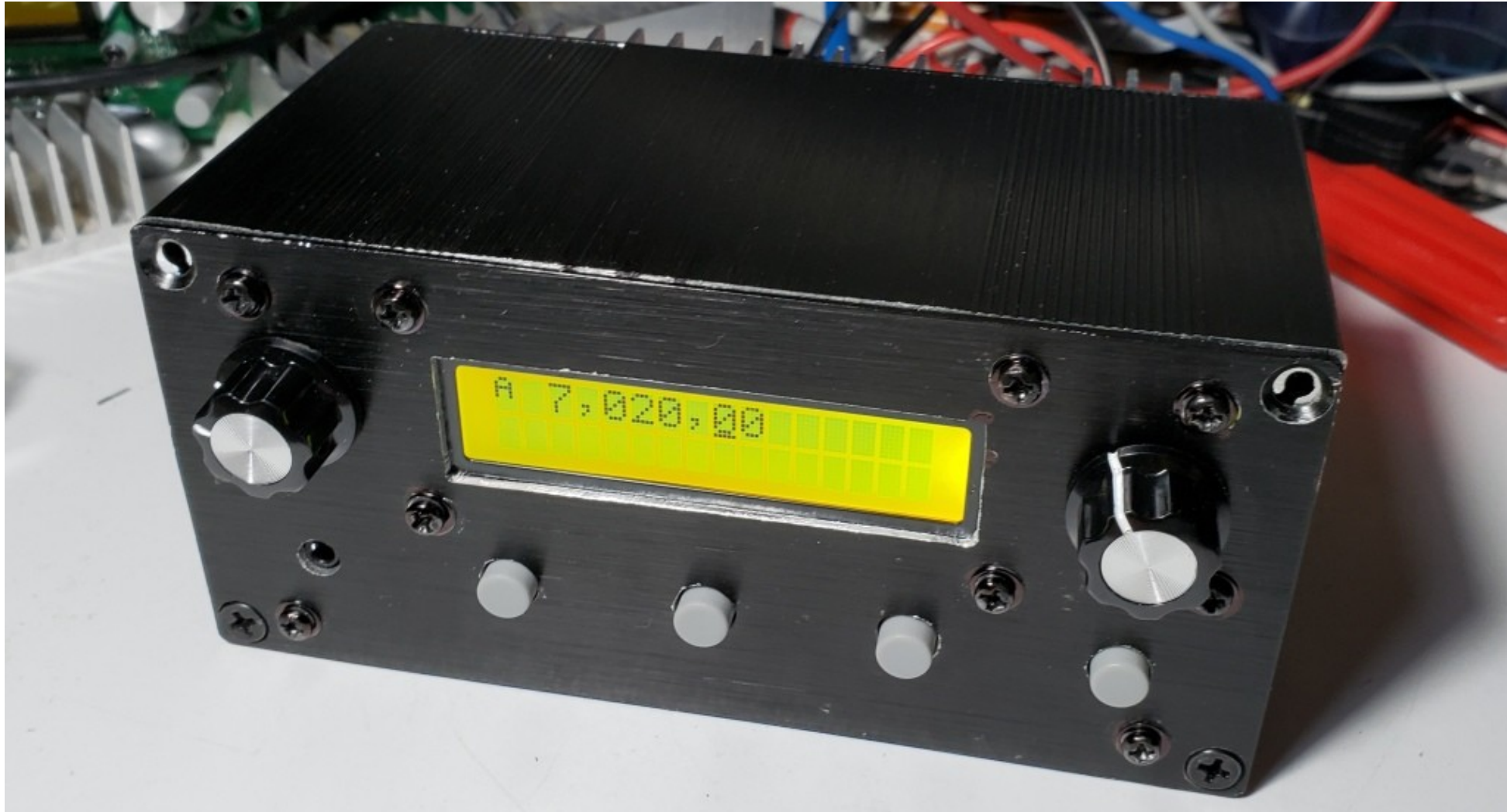


Rear panel connectors

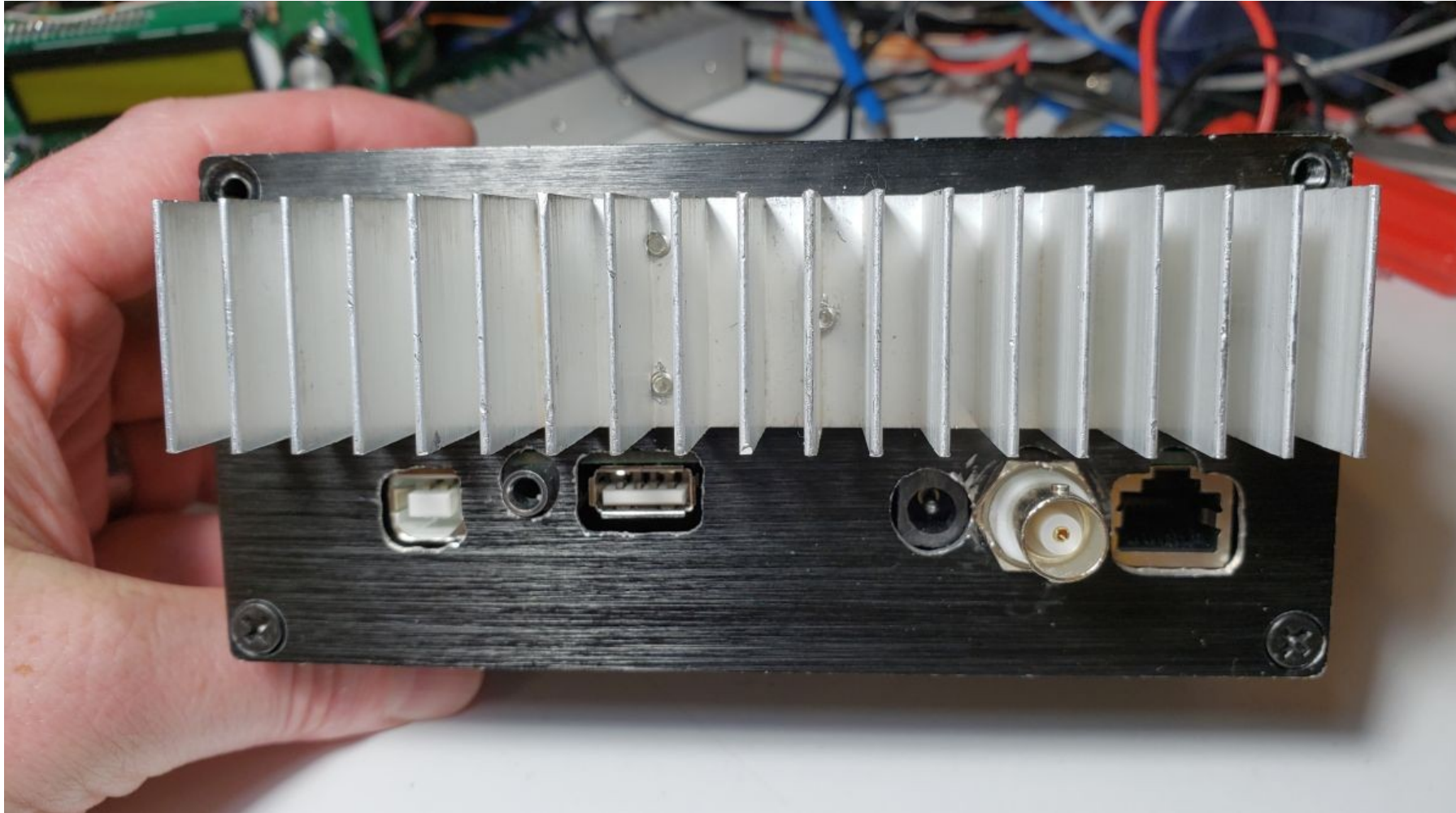


Mechanical and electronic design interact: #1

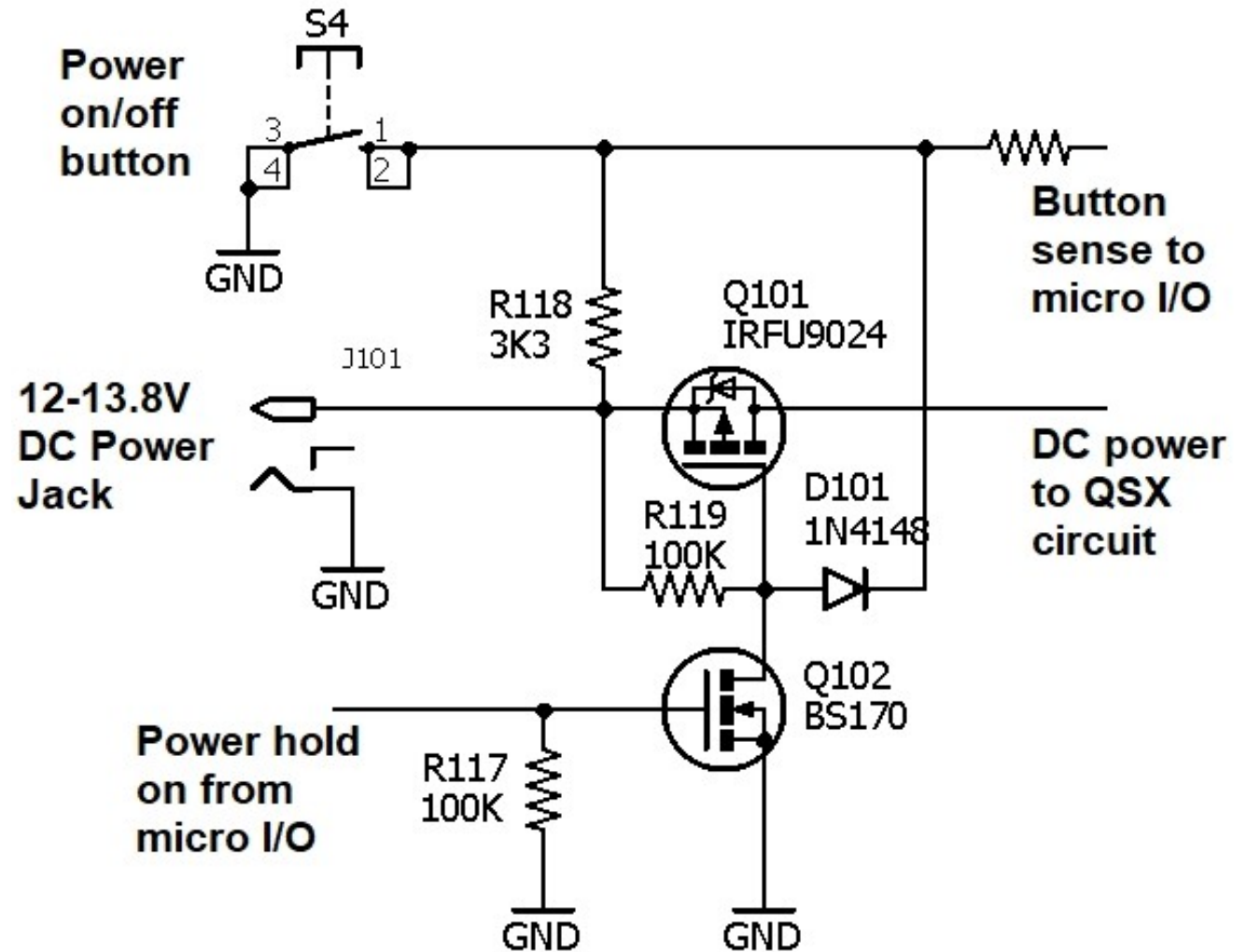- Front panel controls “altitude”
- Reverse polarity protection and soft power switch
- Push button on/off
- Allows “graceful” power-down, saving radio state




Mechanical and electronic design interact: #2

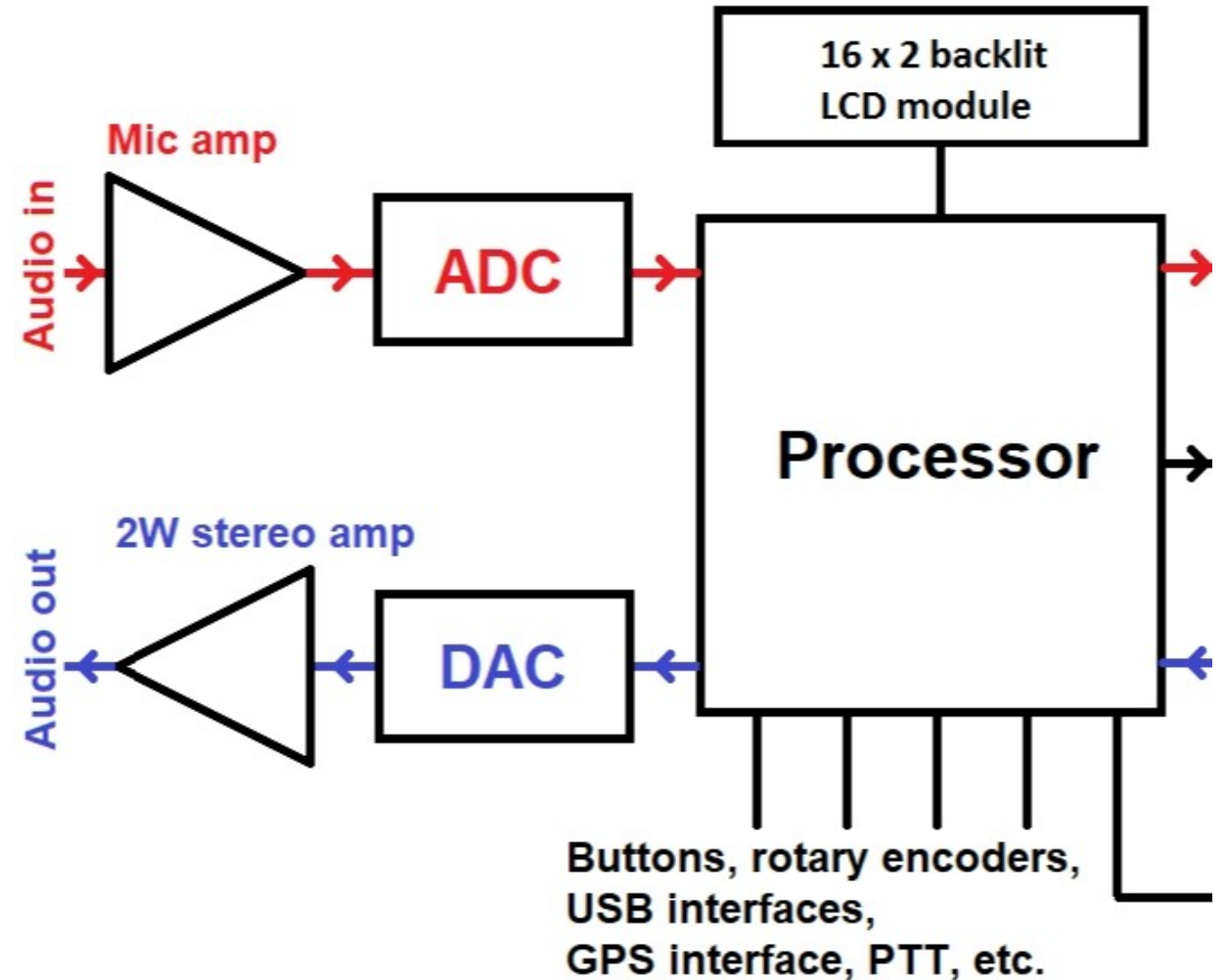- No gain control potentiometer!
- Instead: 24-bit DAC, with rotary encoder
- Plenty of dynamic range!
- Allows “stereo” output
 - Binaural reception
 - Second receiver
 - Volume balance adjustment between left and right ears




ADC and DAC performance

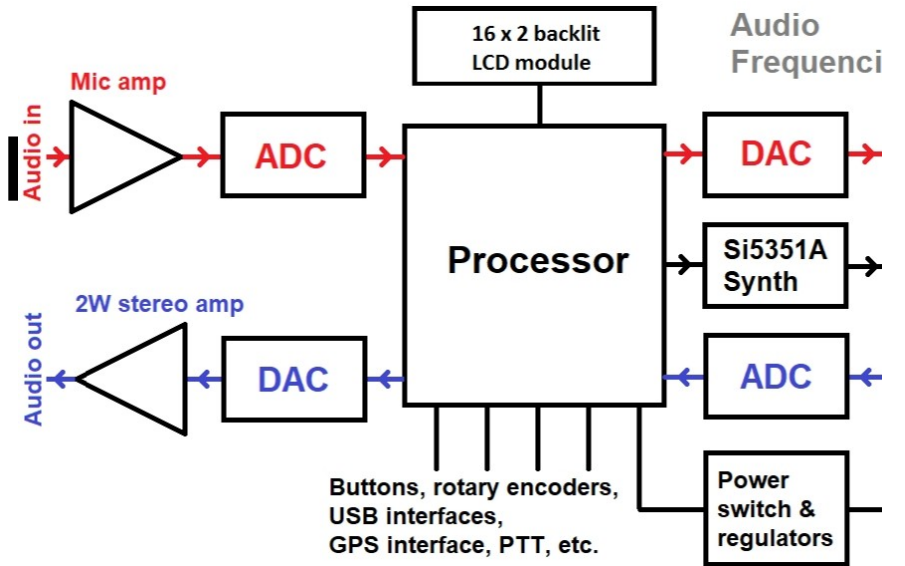


- Four conversions are needed:
 - 12-bit Audio in (microphone)
 - 24-bit Audio out (stereo to earphones)
 - 24-bit ADC input from detector (stereo I & Q channels)
 - 12-bit DAC output to Exciter (stereo I & Q channels)
- 24-bit ADC is critical to performance
 - 6dB per bit theoretical... limited in practice
 - ADC chip has 110dB dynamic range:
- 24-bit audio output DAC, enough dynamic range
- Others can use the internal peripherals of the processor

Qsx 10W Linear PA module

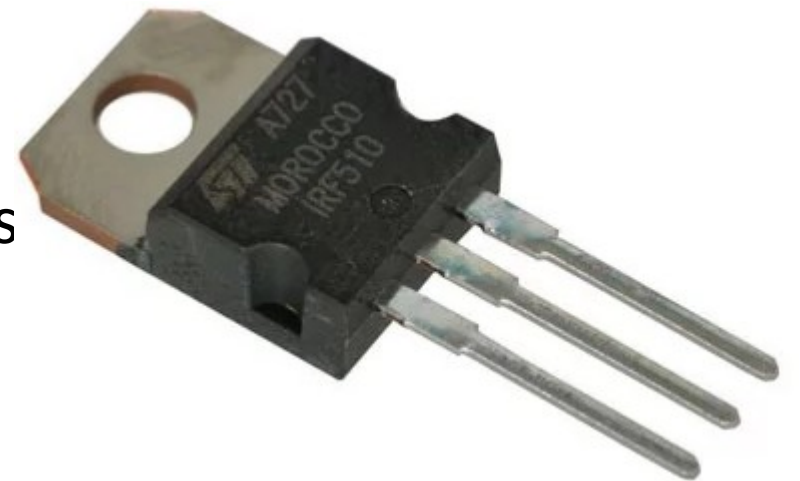
- Relatively massive heatsink allows 100% duty cycle operation at 10W
- Low cost (inexpensive IRF510 MOSFETs)
- 26dB of gain, flat to +/- 1dB across 160m to 10m
- Push-pull BS170 driver, and push-pull IRF510 final, for excellent linearity
- Through-hole plated PCB, all through-hole components (no Surface Mount Devices)
- Standard inexpensive components throughout: eas replaced!
- ROBUST!




Q5X Linear: circuit diagram

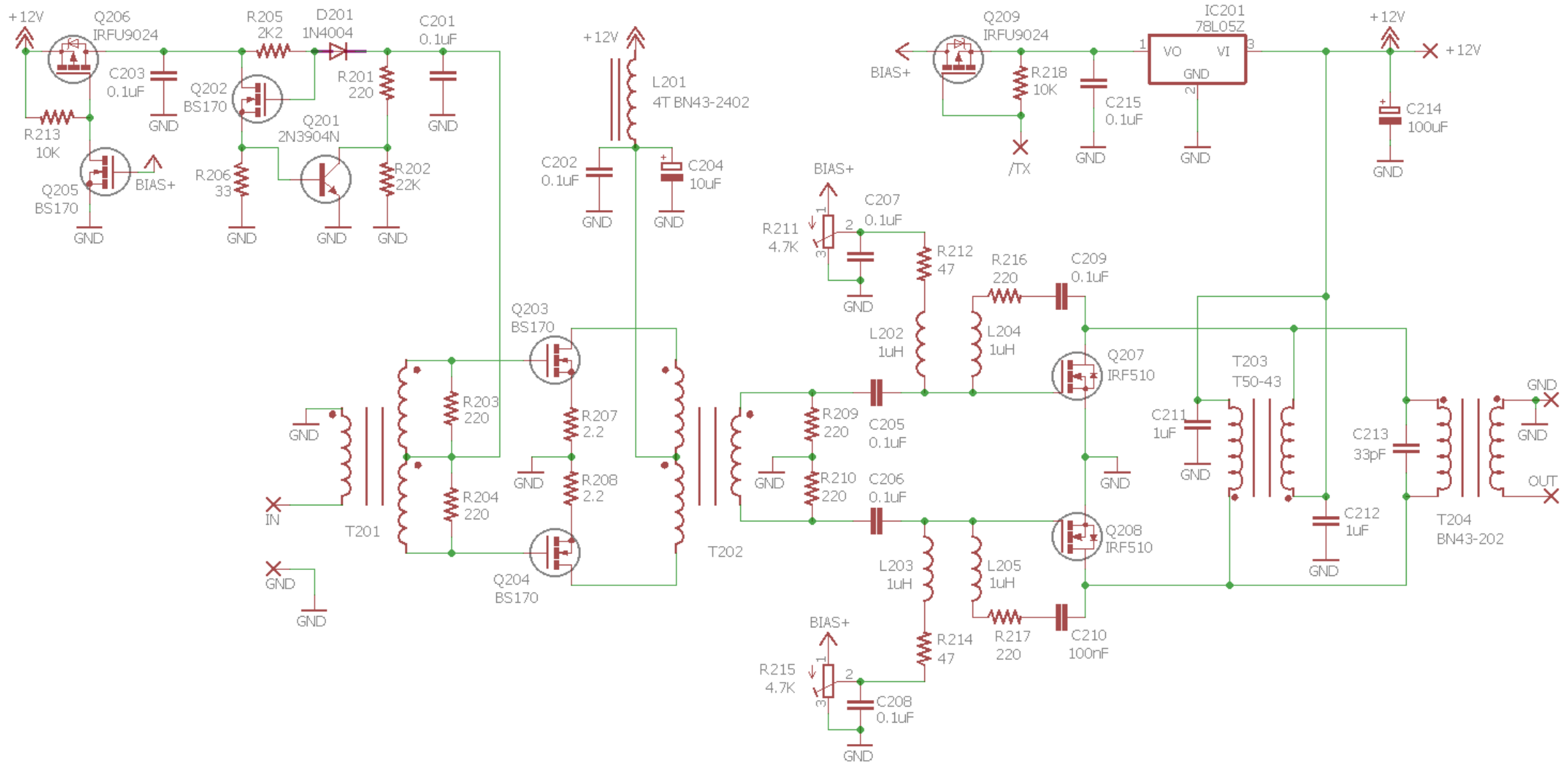

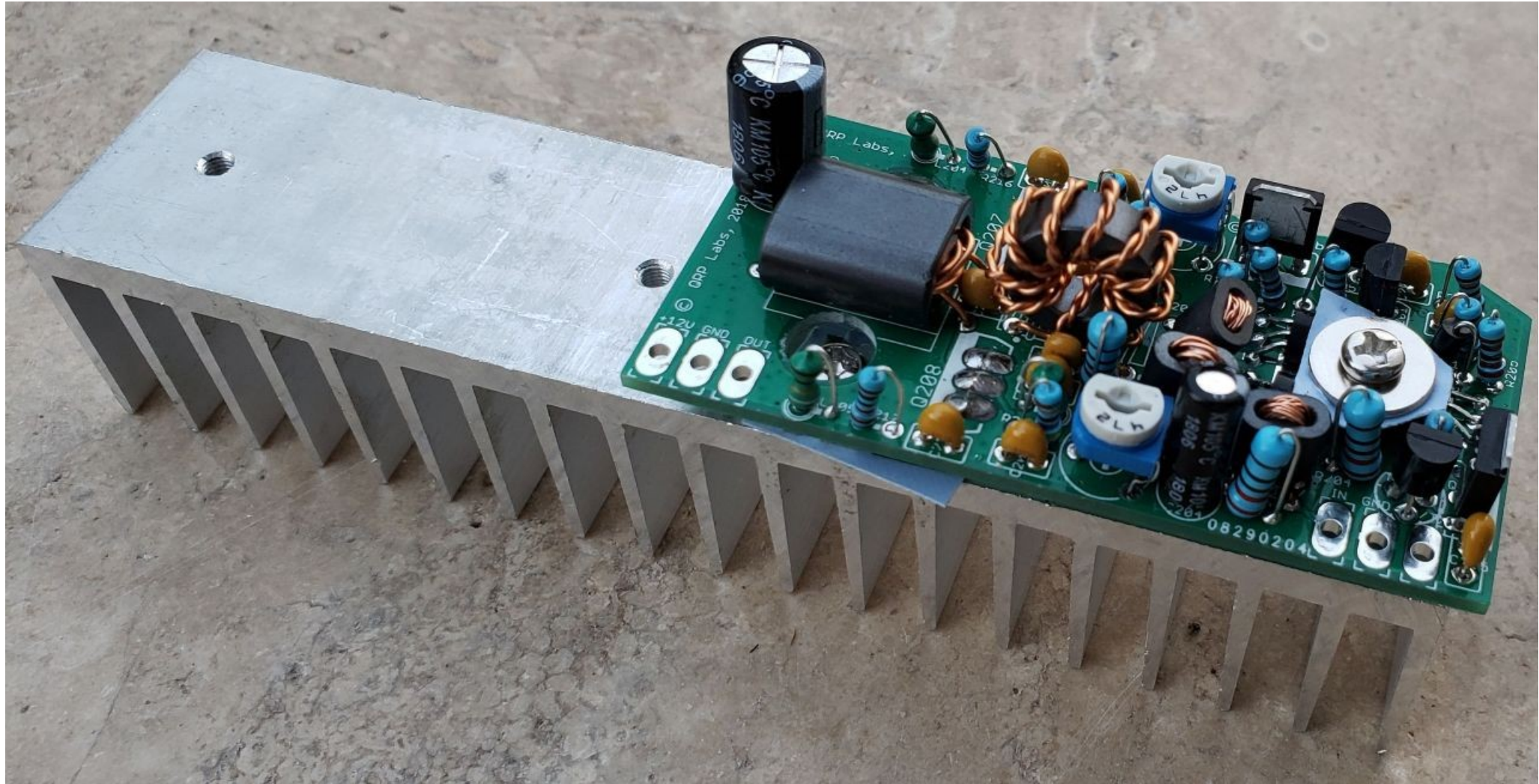
QSX Linear: heatsink 130 x 28mm, 25mm fins



Q5X Linear: symmetric layout

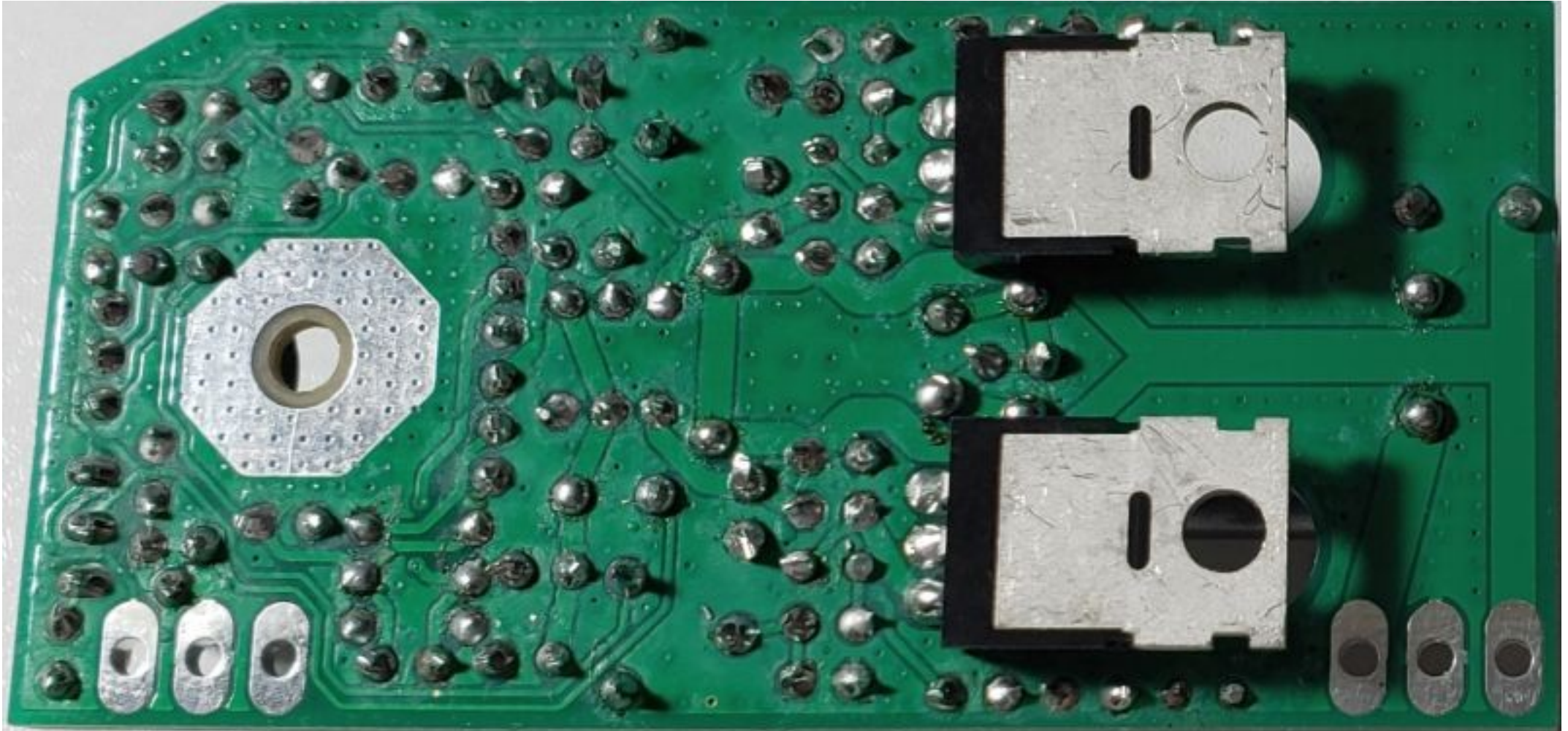


QSX 10W Linear PA module: gain

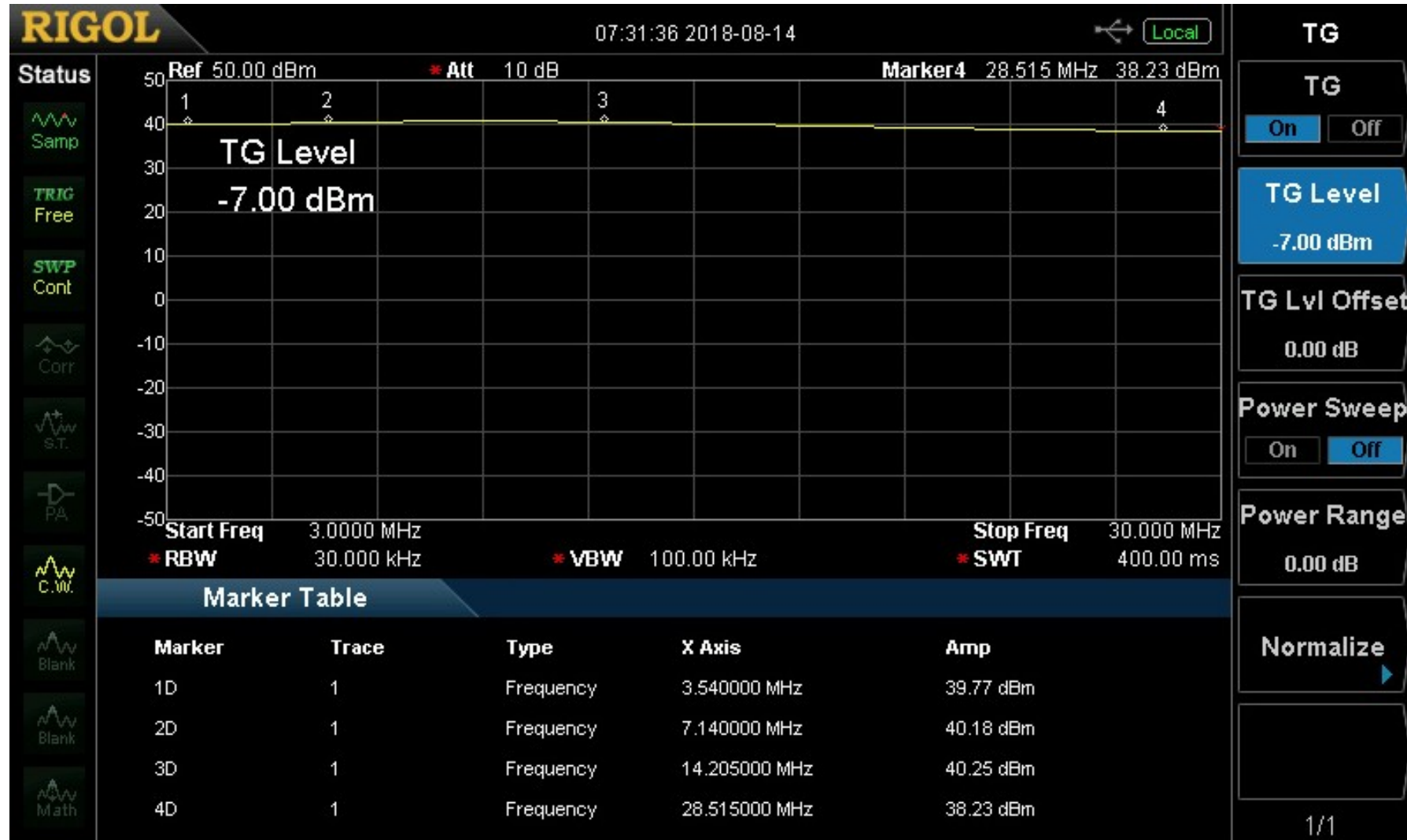



Good intermodulation performance

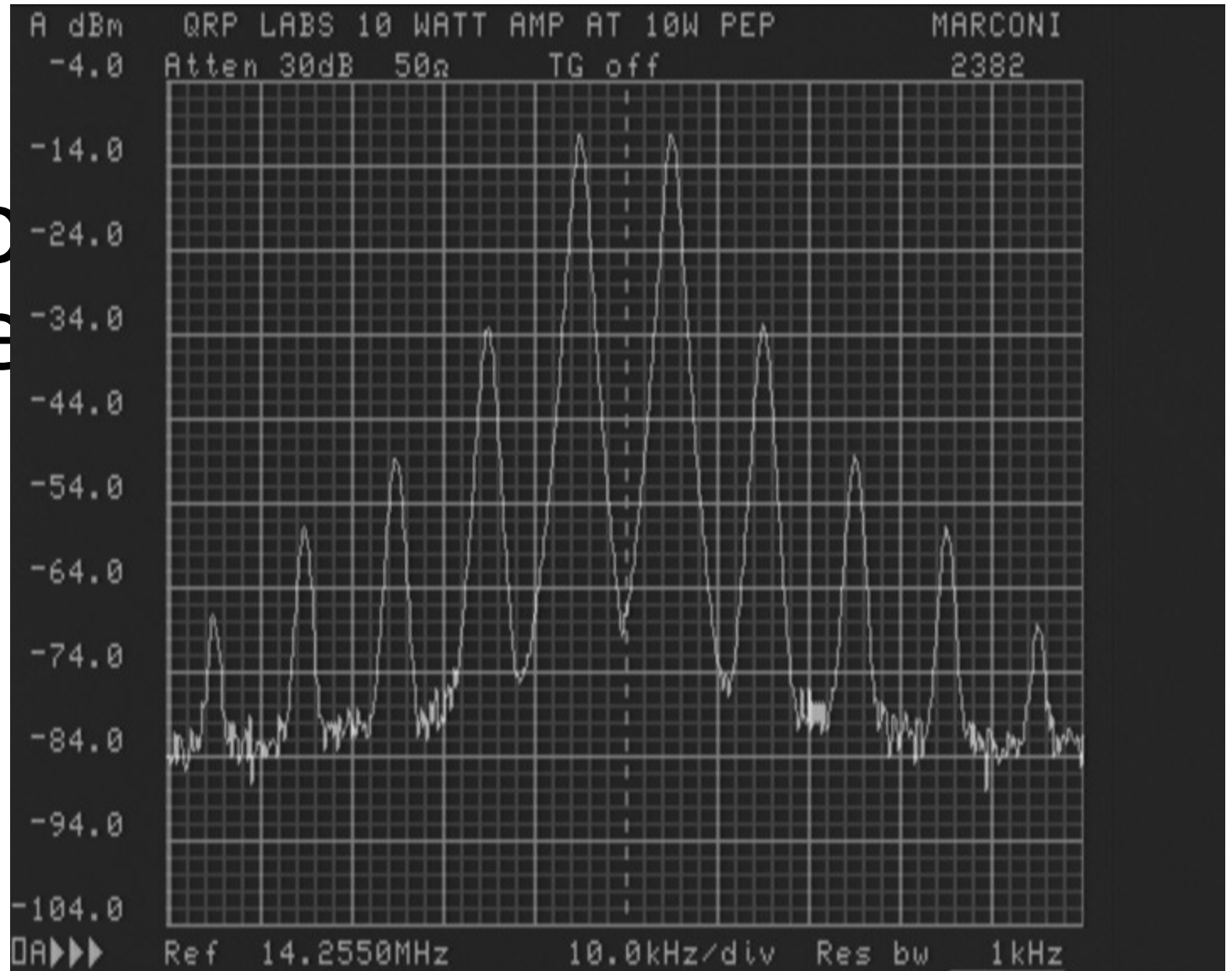- Test on 20m at 12V supply, 10W PEP
- IMD3 -30dB relative to 10W PEP
- IMD5 -45dB
- Predistortion?




Transmit/Receive switch

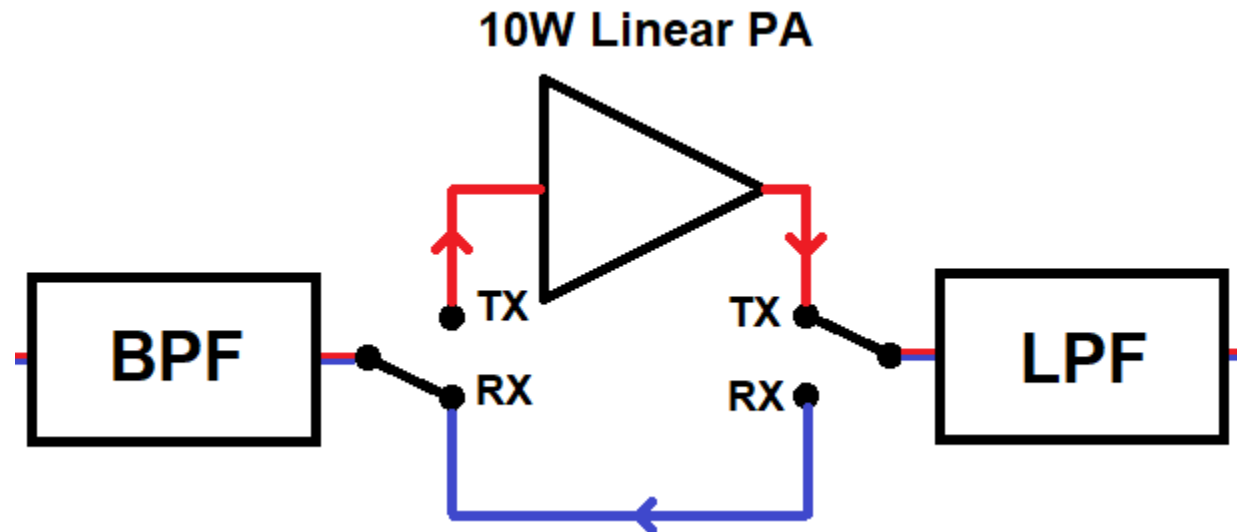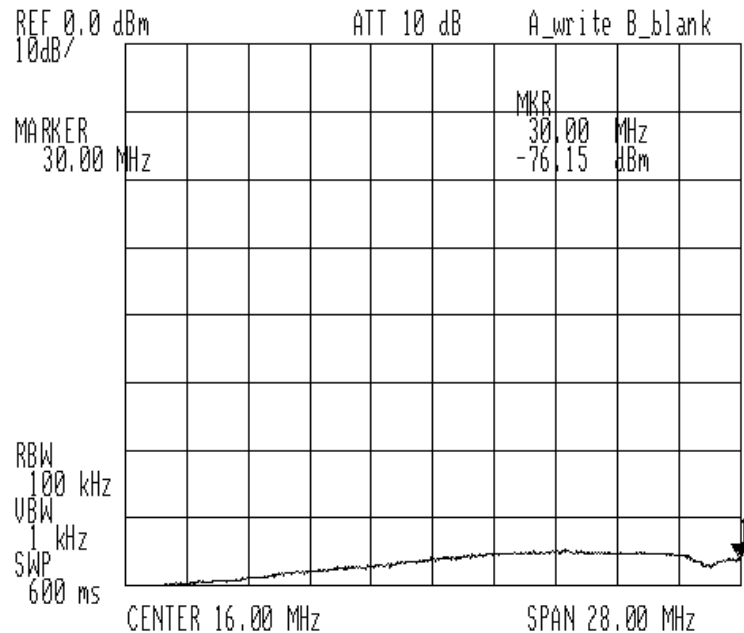- All solid state, no relays: Fast and high performance (CW QSK)
- Low cost, high performance 1N4007 “PIN diode” switch
- RX bypass in “TX” mode has 75+ dB attenuation
- PA output to LPF only 0.1dB insertion loss in TX



PIN diode rules

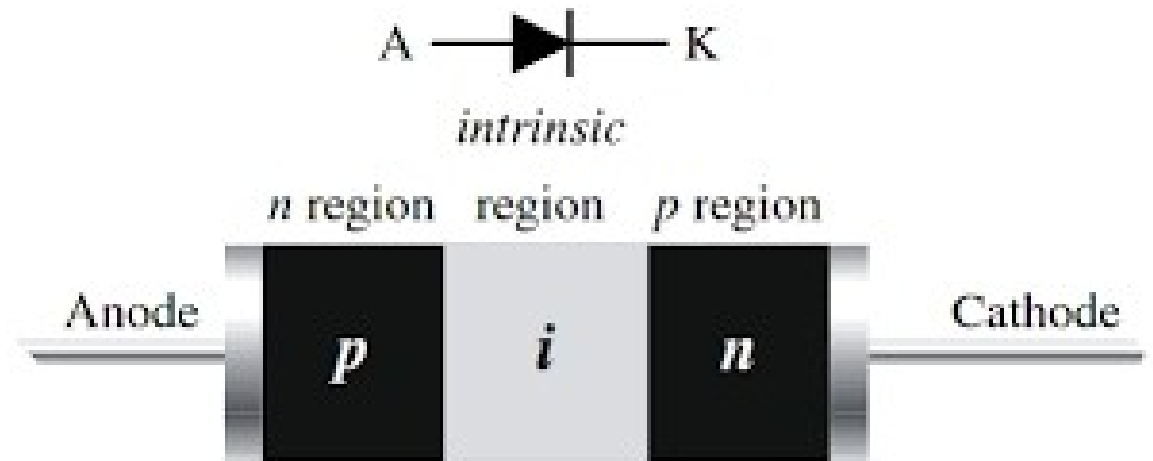
- Real PIN diodes are expensive
- 1N4007 works well as PIN!
- The rules:
- ON requires some forward bias current, 10mA is enough
- OFF requires reverse bias voltage (very little current) higher than the peaks of the RF voltage being blocked



(a) Construction



High performance Tx/Rx switch

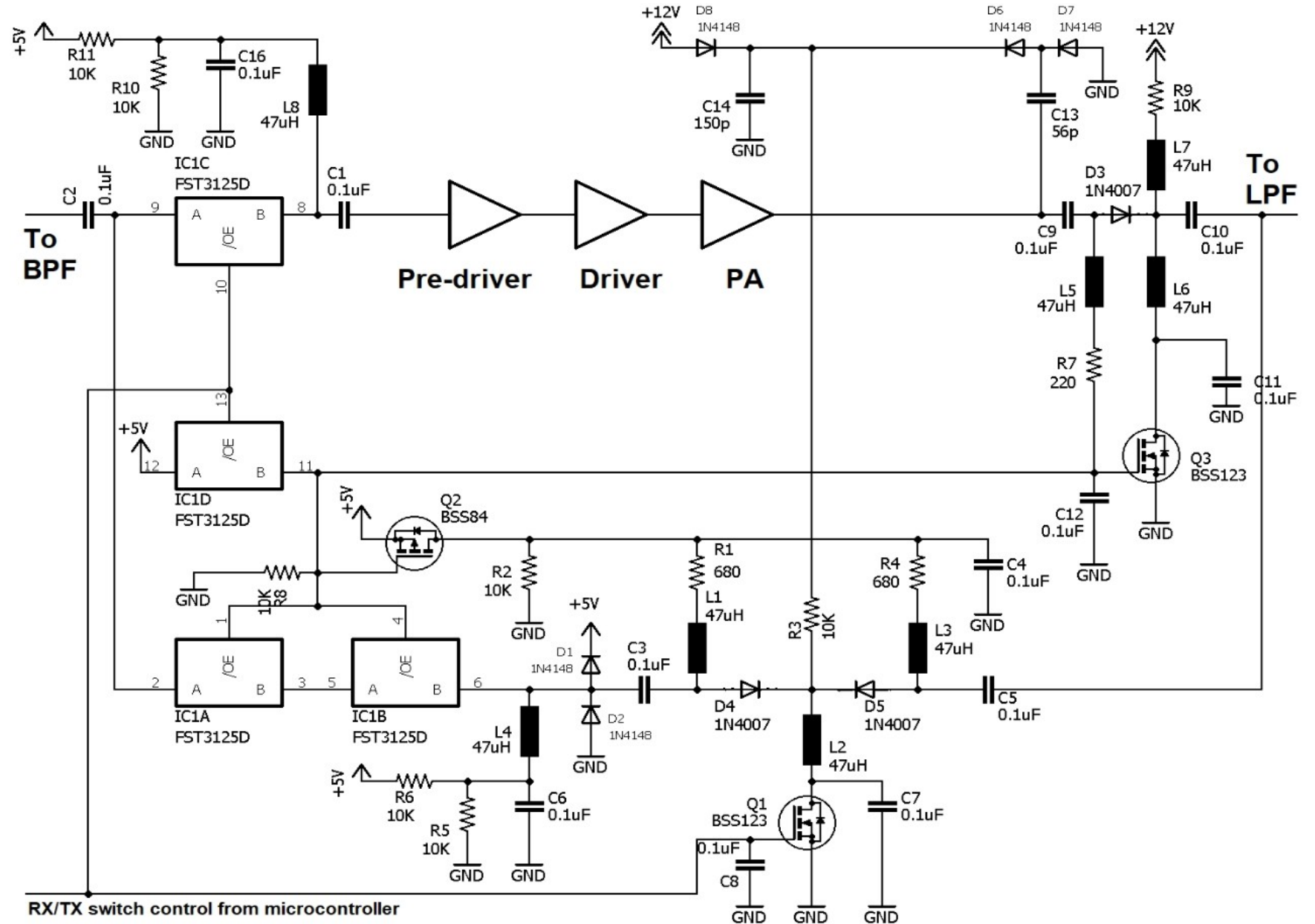

Built-in test equipment


- Signal generator
- frequency counter
- DVM
- Inductance meter
- RF power meter
- SWR
- Spectrum analyzer



Spectrum analyser function for BPF alignment

Display shows:

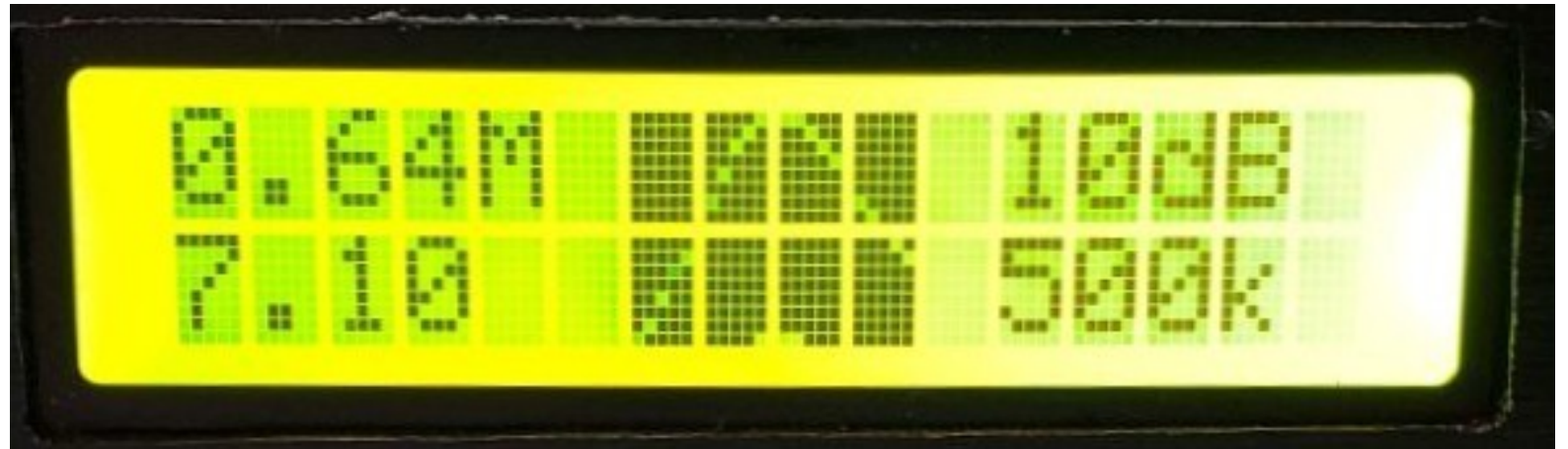- Filter bandwidth
- Center frequency
- Vertical scale (dB/division)
- Horizontal scale (Frequency/division)




Rotary encoder knobs let you adjust center frequency and bandwidth

See YouTube video: <https://www.youtube.com/watch?v=bMoR3Q6gzM>

Weak-signal mode support (standalone, no PC)

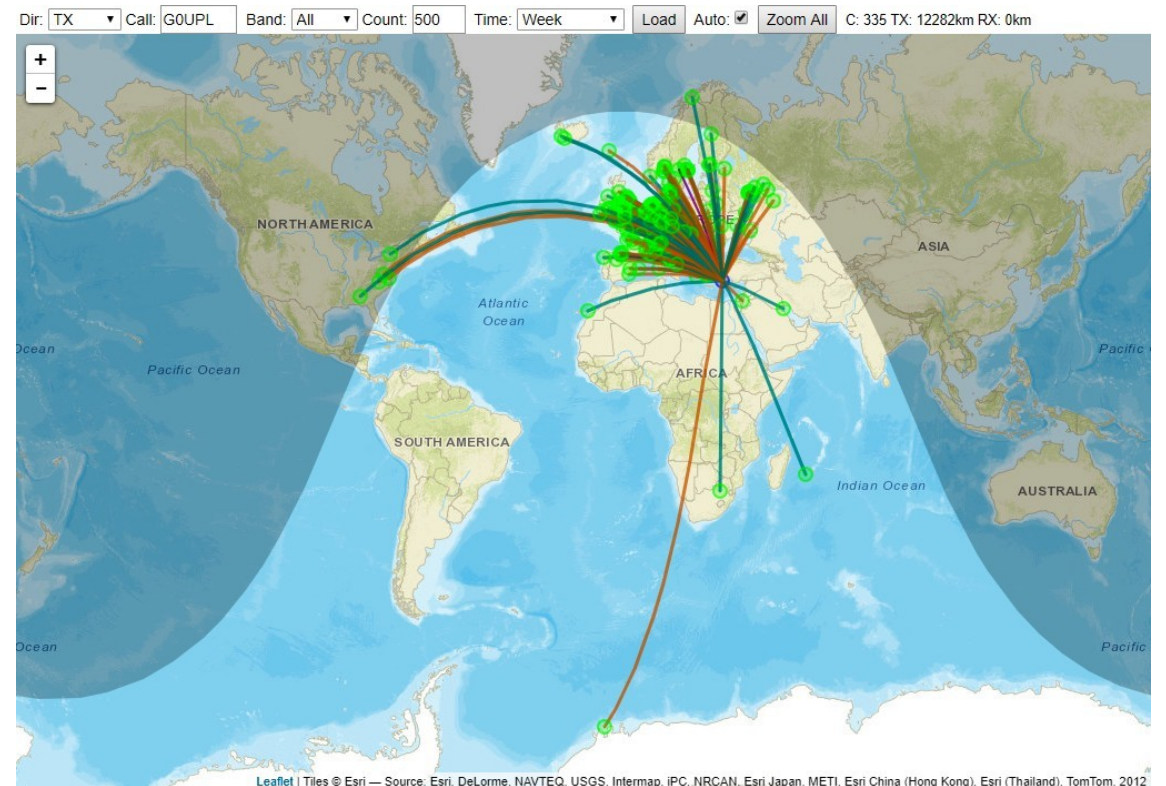
- WSPR (Weak Signal Propagation Reporter)
- CW beacon, RTTY, PSK31
- FT8 beacon
- QRSS modes
(QRSS, FSKCW, DFCW, Slow-Hell)
- Opera
- Pi4
- JT4, JT9, JT65 beacon
- ISCAT (A/B)
- See also Ultimate3S kit
<http://qrp-labs.com/ultimate3/u3s>



SUMMARY – see

<http://qrp-labs.com/qsx>

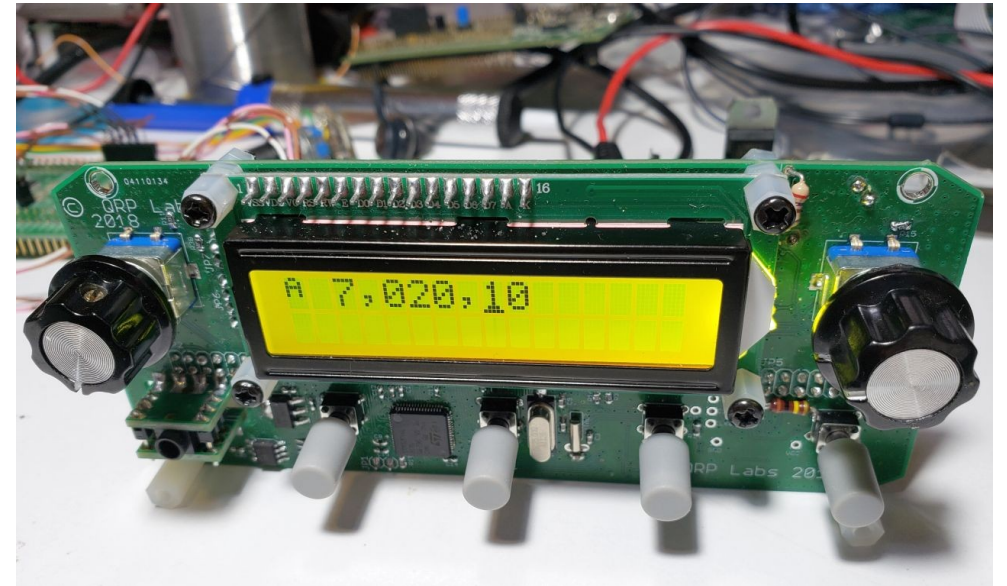- High performance all-band, all-mode 10W HF transceiver
- Fun, flexible educational, customisable
- Performance of a top-range radio at 1/10th the price
- Price target:
 - **\$75** basic 1-band QSX-40
(can also be built for any other single band)
 - **\$150** with all options:
10-band module and aluminium enclosure



QRP Labs

<http://qrp-labs.com>